

CONVERSION FROM SOP TO POS FORM

PRASANTHI VELPULA (FWC22158)

Contents

- 1 PROBLEM
- 2 COMPONENTS
- 3 INTRODUCTION
- 4 TRUTH TABLE
- 5 ARDUINO CONNECTIONS
- 6 CODE

1 PROBLEM

Q.9 A function $F(A, B, C)$ defined by three Boolean variables A, B and C when expressed as sum of products is given by

$F = (\overline{A} \cdot \overline{B} \cdot \overline{C}) + (\overline{A} \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot \overline{C})$ where, \overline{A} , \overline{B} and \overline{C} are the complements of the respective variables. The product of sums (POS) form of the function F is

- (A) $(A + B + C) \cdot (A + \overline{B} + C) \cdot (\overline{A} + B + C)$
- (B) $(\overline{A} + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (A + \overline{B} + \overline{C})$
- (C) $(A + B + \overline{C}) \cdot (A + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + C) \cdot (\overline{A} + \overline{B} + C)$
- (D) $(\overline{A} + \overline{B} + C) \cdot (\overline{A} + B + C) \cdot (A + \overline{B} + C) \cdot (A + B + \overline{C}) \cdot (A + B + C)$

2 COMPONENTS

Component	Value	Quantity
Arduino	Uno	1
Bread board	-	1
Jumper wires	M-M	6
Resistor	1ohms	1
LED	-	1

3 INTRODUCTION

- 1 **SOP Expression** : SOP is useful for representing Boolean expressions as a sum of product terms and it employs minterms which are represented by 'm'. It is formed by considering all of the minterms whose output is HIGH (1) and when minterms are written for SOP, input with value 0 is treated as the input's complement.

- 1 **POS Expression** : POS is useful for representing Boolean expressions as a product of sum terms and it employs maxterms which are represented by 'M'. It is formed by considering all of the max terms whose output is HIGH (0) and When max terms are written for POS, input with value 0 is treated as the variable.

4 TRUTH TABLE

The truth table for the below expression is as follows:
(C) $(A + B + \overline{C}) \cdot (A + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + C) \cdot (\overline{A} + \overline{B} + C)$

A	B	C	F(A,B,C)
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Table 1:

5 ARDUINO CONNECTIONS

- 1. The inputs A, B and C are connected to Arduino D2,D3,D4 pins and output $F(A, B, C)$ is connected to Arduino D5 pin .
- 2. The values for these inputs are conncted either to GND or 5V according to the truth table and the

output pin is connected to anode of LED to display the output, also for limiting current resistor is used.

6 CODE

The Arduino code can be downloaded from the below link :

```
https://github.com/PrasanthiVelpula/FWC\_1/  
tree/main/ide/codes
```